

# B.tech DCLD Lab MCQ test

deysagar3001@gmail.com [Switch account](#)

 Draft saved

## DCLD Lab MCQ test

The inputs of a NAND gate are connected together. The resulting circuit is

- ☐ OR gate
- ☐ AND gate
- ☒ NOT gate
- ☐ None of the above

Clear selection

2's complement of binary number 0101 is .....

- ☒ 1011
- ☐ 1111
- ☐ 1101
- ☐ 1110

Clear selection



An AND gate will function as OR if

- ☐ All the inputs are '0'
- ☐ All the inputs to the gates are "1"
- ☐ Either of the inputs is "1"
- ☒ All the inputs and outputs are complements

Clear selection

Which gates in Digital Circuits are required to convert a NOR-based SR latch to an SR flip-flop?

- ☒ Two 2 input AND gates
- ☐ b) Two 3 input AND gates
- ☐ c) Two 2 input OR gates
- ☐ d) Two 3 input OR gates

Clear selection

NAND. gates are preferred over others because these

- ☐ have lower fabrication area
- ☒ can be used to make any gate
- ☐ consume least electronic power
- ☐ provide maximum density in a chip.

Clear selection



What must be used along with synchronous control inputs to trigger a change in the flip flop?

- ☐ a) 0
- ☐ b) 1
- ☒ c) Clock
- ☐ d) Previous output

Clear selection

What will be the output from a D flip – flop if the clock is low and  $D = 0$ ?

- ☐ 0
- ☒ 1
- ☐ No change
- ☐ Toggle between 0 and 1

Clear selection


What kind of operation occurs in a J – K flip flop when both inputs J and K are equal to 1?

- ☐ a) Preset operation
- ☐ b) Reset operation
- ☐ c) Clear operation
- ☒ d) Toggle operation

Clear selection



 Q30. The circuit of the given figure realizes the function .....



1.  $Y = (\bar{A} + \bar{B}) C + \bar{D} \bar{E}$

2.  $Y = \bar{A} + \bar{B} + \bar{C} + \bar{D} + \bar{E}$

☒ Option 1

☐ Option 2

☐  $AB + C + DE$

☐  $AB + C(D + E)$

Clear selection

The basic storage element in a digital system is .....

☒ flipflop

☐ counter

☐ multiplexer

☐ encoder

Clear selection

Back

Submit

Clear form

# Google Forms

