

EXPT NO.7 :

STUDY OF MULTIPLEXER

Objective :

To study the multiplexer.

Equipments :


Logic Circuit Simulator Pro.

Theory :

Multiplexer :



Multiplexer means transmitting a large number of information units over a smaller number of channels or lines.


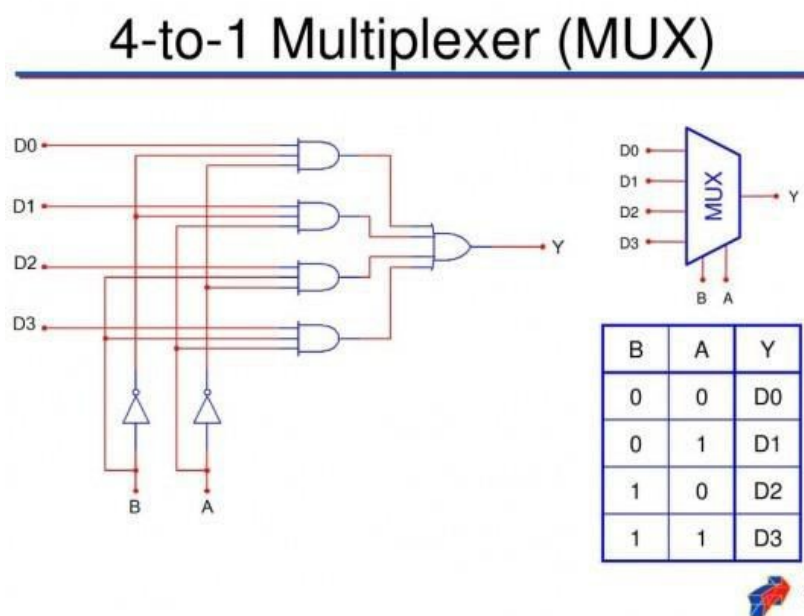
A multiplexer is a combinational logic circuit that selects binary information from one of many input lines and directs it to a single output line. The selection of a particular input line is controlled by a set of selection lines, whose bit combination determines which input is selected.



Procedure :

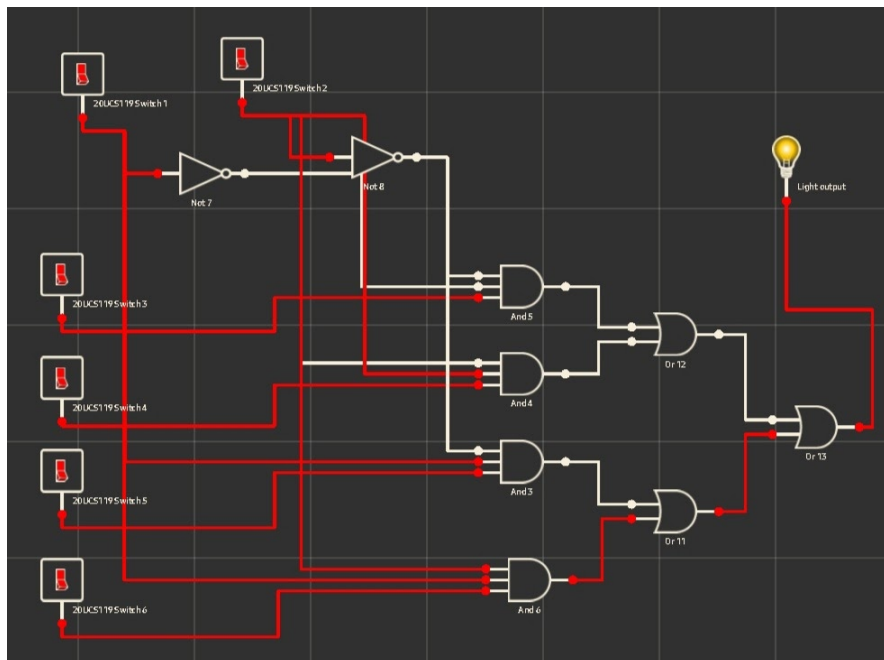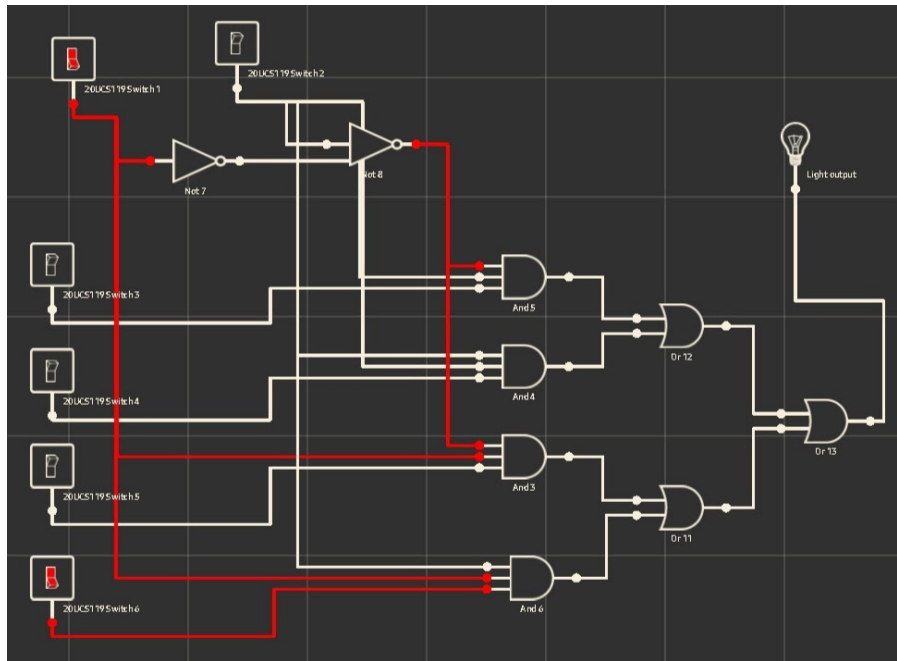- Do the connections as shown and switch on the power supply.
- Apply proper logic inputs on the multiplexer and observe the output on LEDs.
- Verify the function table of the multiplexer in both the cases.



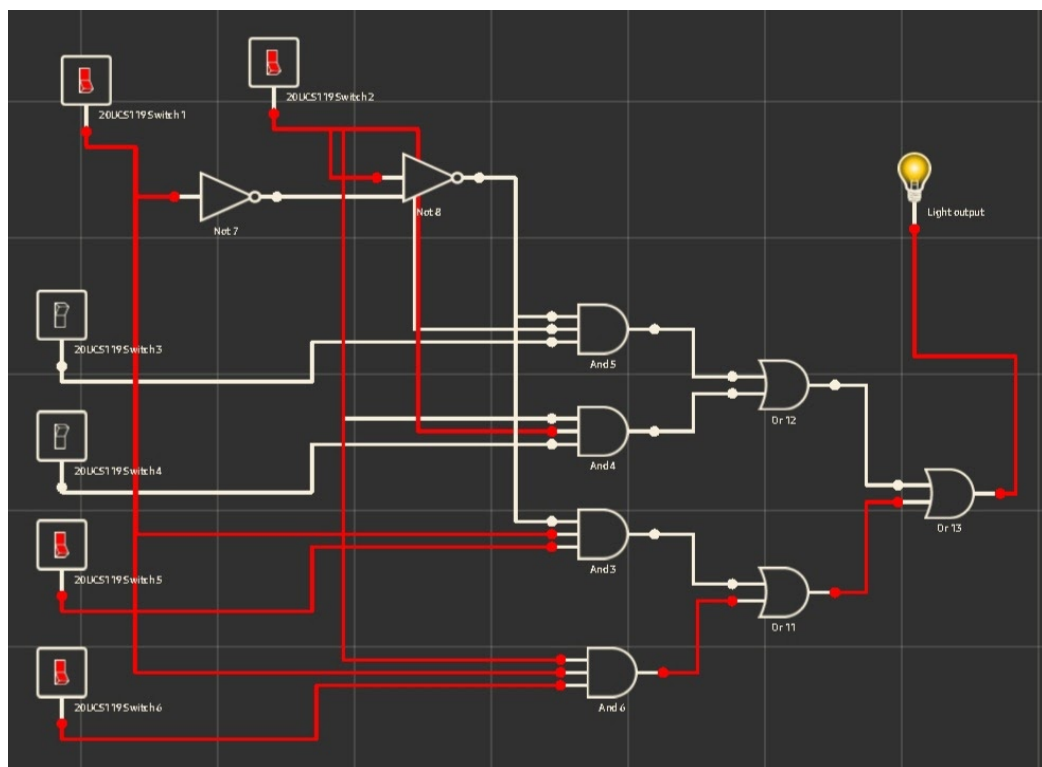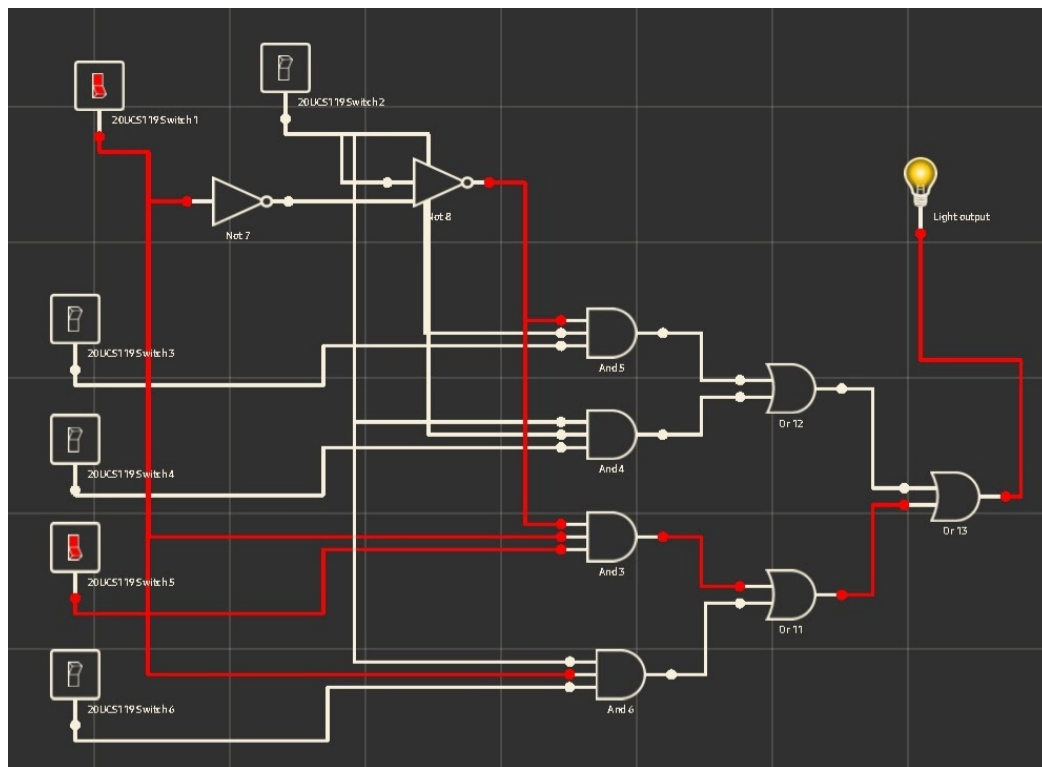

TRUTH TABLE:

| Select Data Inputs | | Output |
|--------------------|-------|--------|
| S_1 | S_0 | Y |
| 0 | 0 | D_0 |
| 0 | 1 | D_1 |
| 1 | 0 | D_2 |
| 1 | 1 | D_3 |

Conclusion :

Hence the functionality of Multiplexer is verified.