

SET-1

- 1) Implement and Verify De Morgan's Law.
- 2) Implement and Verify half adder using NAND Gate.

SET-2

- 1) Implement and Verify Full adder using NAND Gate.
- 2) Simplify the following Boolean Expression
 - i) $AB(A+B)(B+B)$

SET-3

- 1) Implement and Verify Full Sub-tractor.
- 2) Simplify the following Boolean Expression
 - i) $(A+C)(AD+AD)+AC+C$

SET-4

- 1) Implement and Verify Full Sub-tractor.
- 2) Simplify the following Boolean Expression
 - i) $A(A+B)+(B+AA)(A+B)$

SET-5

- 1) Implement and Verify Multiplexer.

SET-6

- 1) Implement and Verify Full Sub-tractor.
- 2) Simplify the following Boolean Expression
 - i) $A(A+B)+(B+AA)(A+B)$

SET-7

- 1) Implement and Verify De Morgan's Law.
- 2) Simplify the following Boolean Expression
 - i) $Y+X(Y+Z)+Y(Y+Z)$

SET-8

- 1) Implement and Verify Half Sub-tractor.
- 2) Simplify the following Boolean Expression
 - i) $x * y * z + x * z$

SET-9

- 1) Implement the Boolean expression simplification-
 $AB(A+B)(B+B)$
- 2) Implement and verify Full Sub-Tractor.

SET-10

- 1) Implement the Boolean expression simplification-
 $AB(A+B)(B+B)$
- 3) Implement and Verify Half Sub-tractor.

SET-11

- 1) Implement and verify Full Sub-Tractor.
- 2) Simplify the flowing Boolean Expression
 $Y + X(Y + Z) + Y(Y + Z)$

SET-12

- 1) Implement and Verify Full adder using NAND Gate.
- 2) Simplify the flowing Boolean Expression
 $Y + X(Y + Z) + Y(Y + Z)$