

DIGITAL LOGIC AND CIRCUIT DESIGN LAB
LABORATORY ASSIGNMENTS
3rd SEMESTER COMPUTER SCIENCE & ENGINEERING



SUBMITTED BY

NAME : ADITYA KIRAN PAL

SECTION : A

ENROLLMENT NO : 20UCS119

REGISTRATION NO : 2012709

SUBJECT : DCLD LAB

SEMESTER & YEAR : 3rd SEM , 2nd YEAR B. Tech.

DEPARTMENT OF COMPUTER SCIENCE & ENGINEERING
NATIONAL INSTITUTE OF TECHNOLOGY, AGARTALA
Jirania PO, Agartala, Barjala, Tripura-799046

INDEX

[illegible]

EXPT NO.3 :

STUDY OF DE-MORGAN'S THEOREM

Objective :

To study and verify de-morgan's theorem.

Equipments :

Logic Circuit Simulator Pro.

Theory :

A mathematician named DeMorgan developed a pair of rules regarding group complementation in Boolean algebra. By group complementation, represented by a long bar over more than one variable.

Inverting all inputs to a gate reverses that gate's essential function from AND to OR, or vice versa, and also inverts the output. So, an OR gate with all inputs inverted (a Negative-OR gate) behaves the same as a NAND gate and an AND gate with all inputs inverted (a Negative-AND gate) behaves the same as a NOR gate. This theorems states the same equivalence in "backward" from: that inverting the output of any gate results in the same function as the opposite type of gate (AND vs OR) with inverted inputs :

A long bar extending over the term AB acts as a grouping symbol, and as such is entirely different from the product of A and B independently inverted. In other words, $(AB)'$ is not equal to $A'B'$. Because the "prime" symbol ($'$) cannot be stretched over two variables like a bar can, we are forced to use parentheses to make it apply to the whole term AB in the previous sentence. A bar, however, acts as its own grouping symbol when stretched over more than one variable. This has a profound impact on how Boolean expressions are evaluated and reduced, as we shall see.

De Morgan's theorem may be thought of in terms of breaking a long bar symbol. When a long bar is broken, the operation directly underneath the break changes from addition to multiplication, or vice versa, and the broken bar pieces remain over the individual variables

Procedure :**THEOREM 1:** $\overline{AB} = \overline{A} + \overline{B}$

1. Do the connection as shown in the figure.
2. Connect A & B terminals to the logic inputs from input switches.
3. Connect both the outputs to led indicators in the Output section.
4. Provide different combinations of inputs A & B and observe the output on LEDs to verify the theorem.

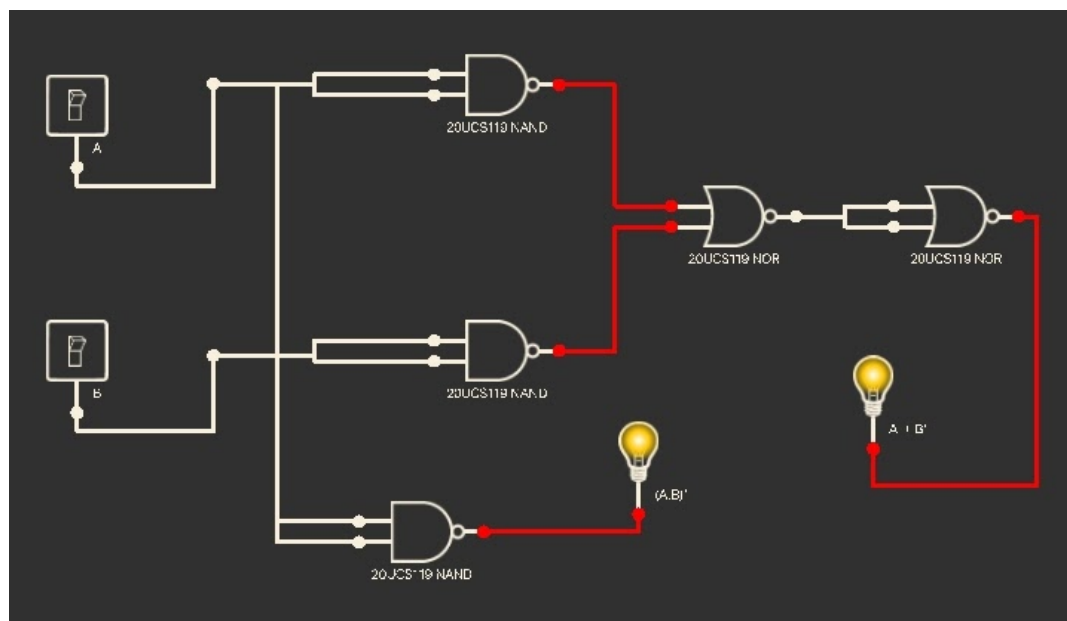
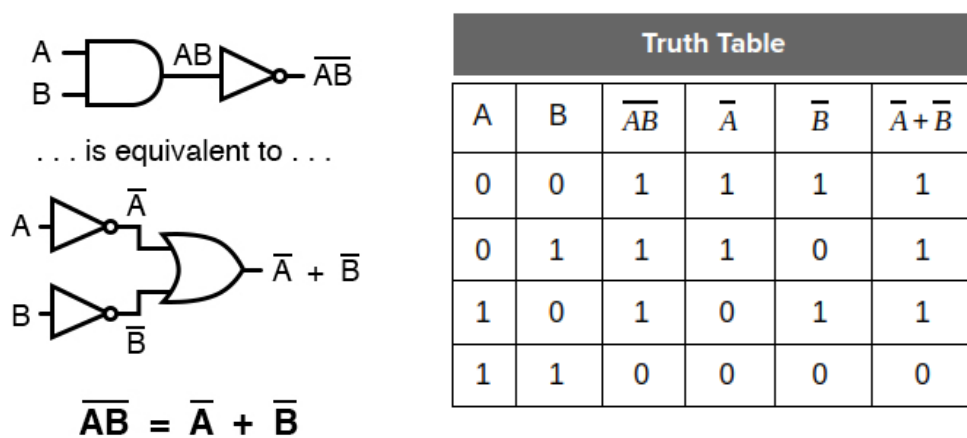


Figure : $\overline{AB} = \overline{A} + \overline{B}$

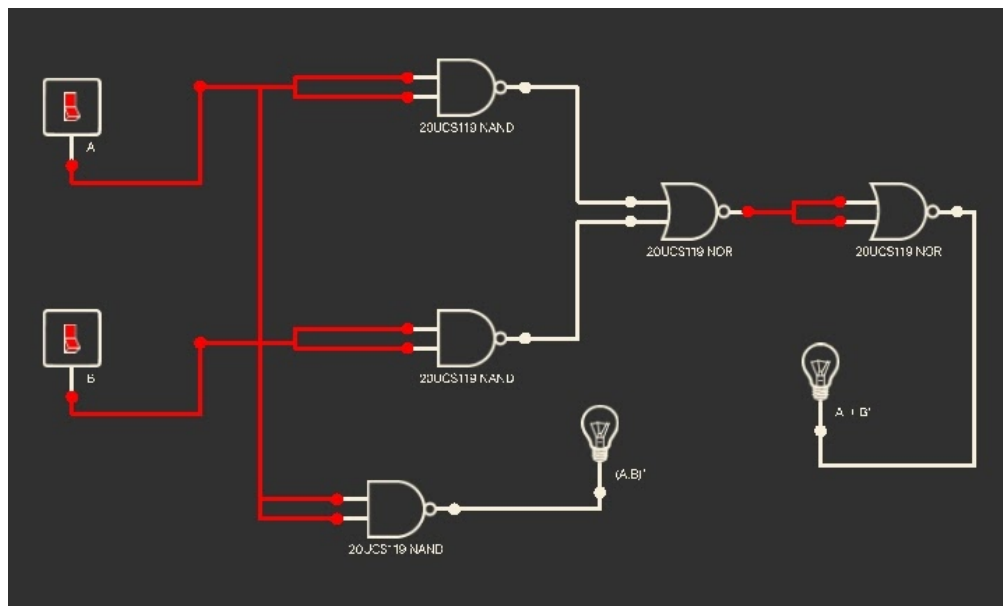


Figure : $\overline{AB} = \overline{A} + \overline{B}$


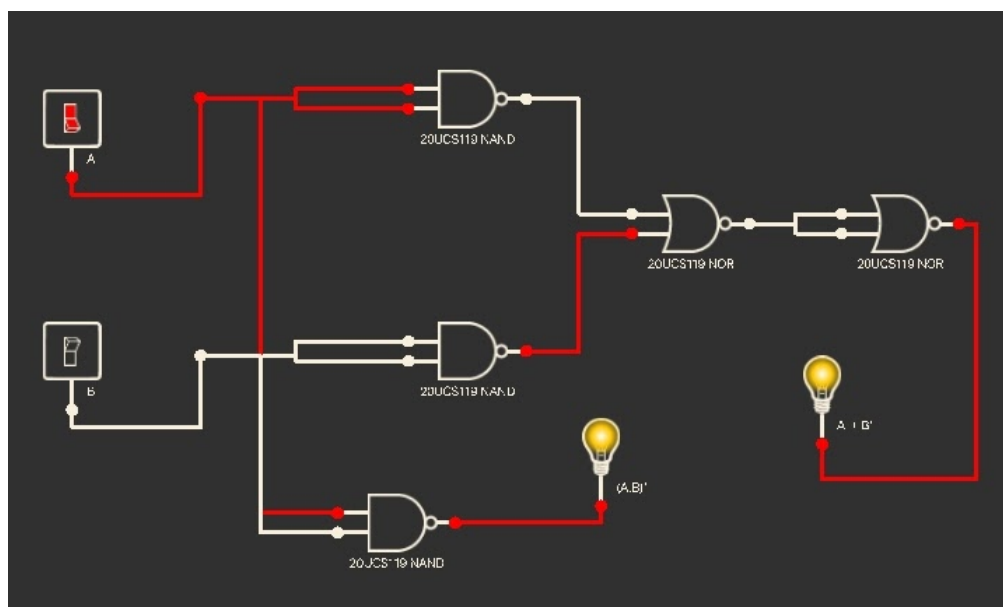



Figure : $\overline{AB} = \overline{A} + \overline{B}$

THEOREM 2 : $\overline{A+B} = \bar{A} \cdot \bar{B}$

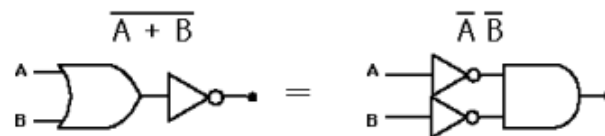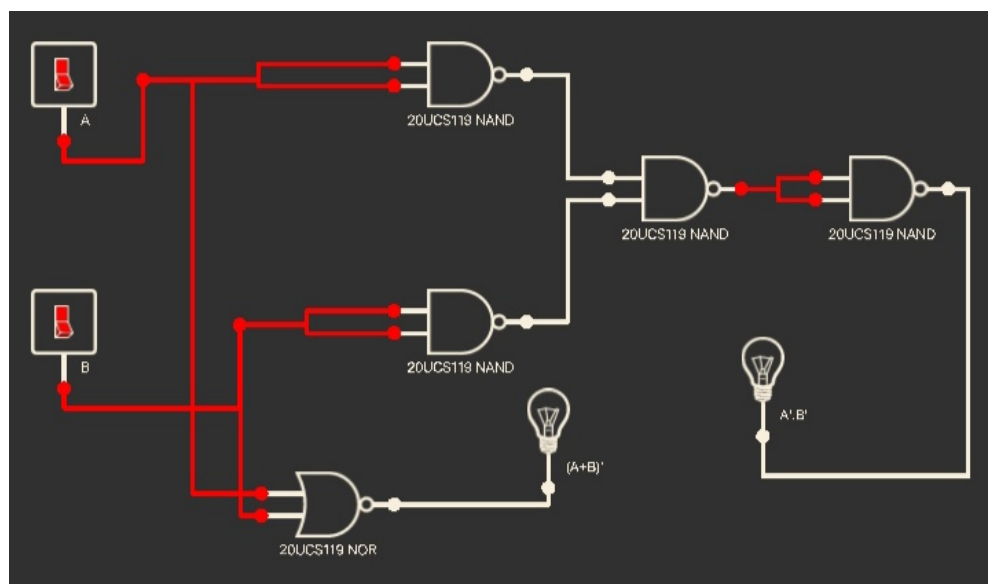1. Do the connection as shown in the figure.
2. Connect A & B terminals to the logic inputs from input switches.
3. Connect both the outputs to led indicators in the Output section.
4. Provide different combinations of inputs A &B and observe the output on LEDs to verify the theorem.



Truth Table						
A	B	\bar{A}	\bar{B}	A+B	$\overline{A+B}$	$\bar{A} \cdot \bar{B}$
0	0	1	1	0	1	1
0	1	1	0	1	0	0
1	0	0	1	1	0	0
1	1	0	0	1	0	0

**Figure :** $\overline{A+B} = \bar{A} \cdot \bar{B}$

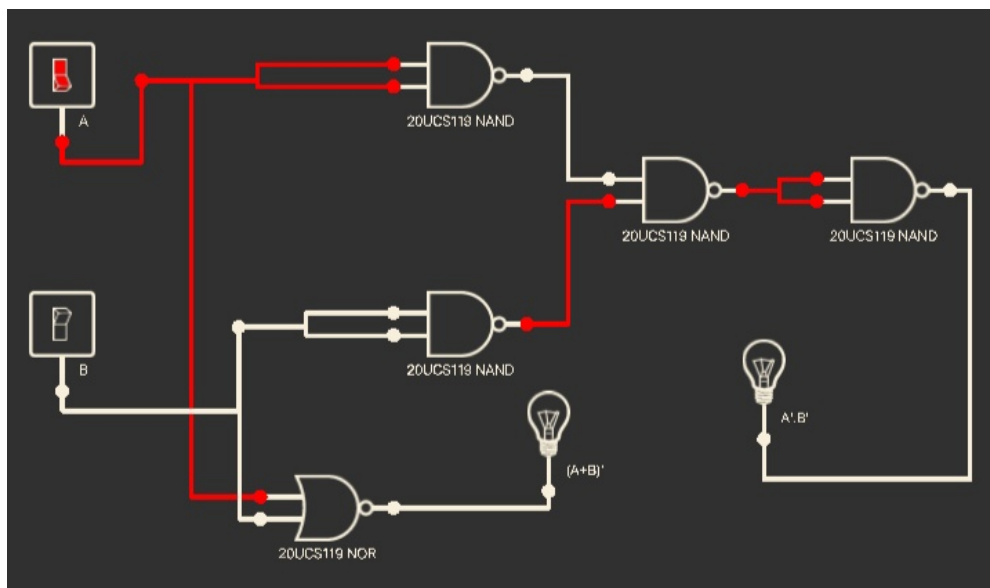


Figure : $\overline{A+B} = \overline{A} \cdot \overline{B}$

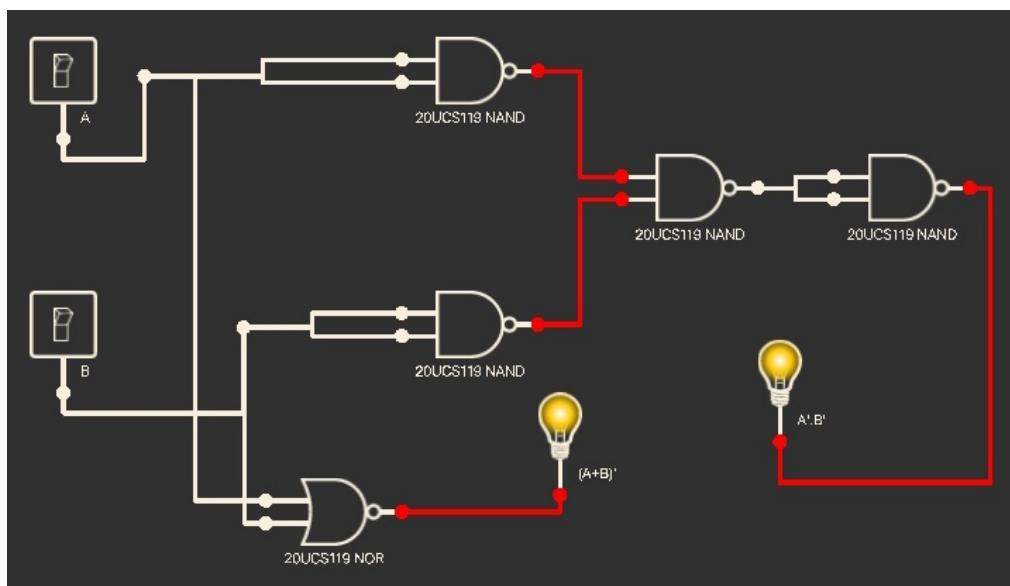


Figure : $\overline{A+B} = \overline{A} \cdot \overline{B}$

Conclusion :

Hence, De-Morgan's theorem is verified.